

System Synthesis and Modeling (CSCE 3953)

Final Project (Step 2) Report

Zack Fravel

11/9/16

zpfravel@uark.edu

Report

Step 2 of the project had us design, simulate, and synthesize our register components as well as the program counter for our RISC microprocessor. I looked at the configuration of our system and determined to break this up into four separate modules. The memory address register (MAR) checks if an enable signal is active, if so it latches the data from the bus into its register and continuously outputs its contents to the memory. The memory data register (MDR) is a little more complicated in that it requires two registers internally, one for reading and one for writing to/from memory. So, I have three enable signals, one for reading, writing, and outputting to the bus. When the read signal is high, the register latches in the data it is receiving from memory. When the output enable signal is active, it sends this data through a tri state to the bus. Whenever write enable is active, the other internal register latches the data from the bus and continuously outputs its data to the memory. Finally, the general purpose register (GPR) is a simple read/write register. I have an in-enable signal to allow the register to latch data from the bus, and an out-enable signal to allow the tri state buffer to send the register's contents across the bus. All of these registers also check for signal reset and set their contents to 16'h0000.


Last but not least there is the program counter. The program counter is very simple, on reset it sets its internal register to 16'h0000. The counter continuously checks for an increment signal that is generated from the FSM's in the decoding process, upon increment == 1 the counter increments its value by one. Its output is also gated by a tri state buffer. All designs were synthesized successfully, I have included screenshots of delay.


Source Code/Screenshots/Testbench

MAR

```
1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Final Project (Step 2)
4
5 module MAR(clk, reset, data_in, enI, data_out);
6
7 // Input/Output/Register Declaration
8 input clk; input reset; input[15:0] data_in;
9 input enI; output[15:0] data_out;
10 reg[15:0] data;
11
12 // Architecture
13
14 always@(posedge clk or posedge reset)
15 begin
16     if (reset == 1)
17         begin
18             data <= 16'h0000;
19         end
20     else
21         if (enI == 1)
22             data <= data_in;
23         end
24
25     assign data_out = data;
26 end
27 endmodule
```

```
// Zack Fravel
// System Synthesis and Modeling
// Final Project (Step 2)
`timescale 1ns/1ns
module MAR_tb;
// Inputs
    reg clk; reg reset; reg[15:0] bus_in; reg enI;
// Outputs
    wire data_out;
// Declare module
    MAR test(clk, reset, bus_in, enI, data_out);
// Testbench
    always #10 clk = ~clk;
    initial
    begin
        clk = 0; reset = 0; bus_in = 16'h0000; enI = 0;
        #20; reset = 1;
        #20; reset = 0;
        #40; bus_in = 16'h1111;
        #20; enI = 1;
        #20; enI = 0;
    end
endmodule
```

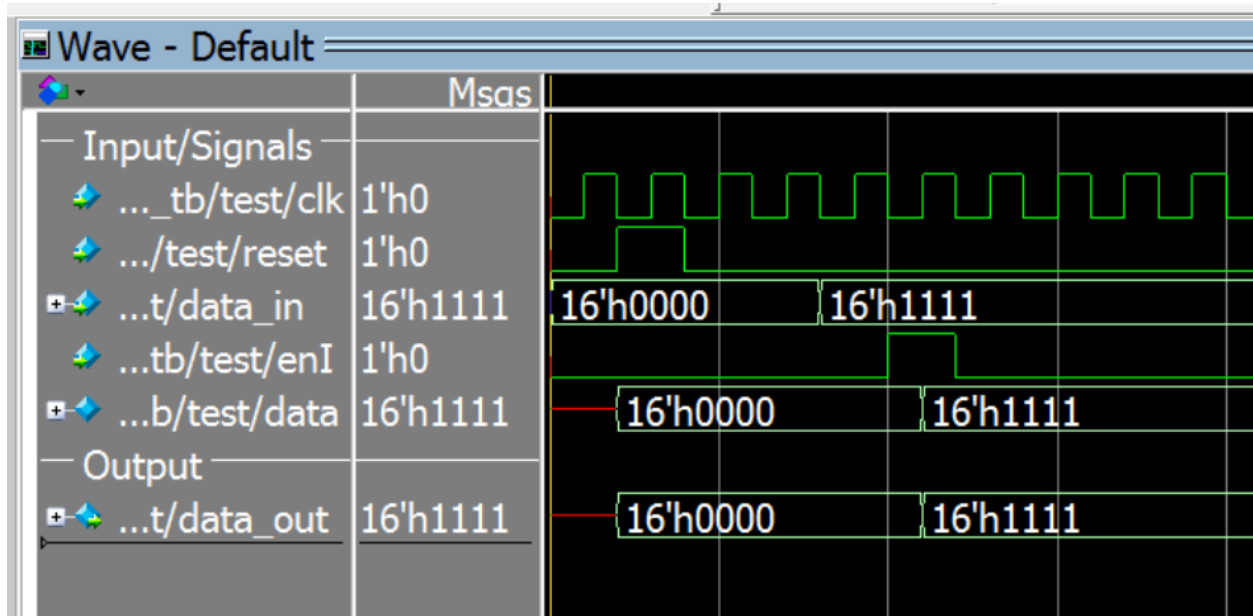

 

MDR

ers/Meryl/Documents/System Synthesis and Modeling/Final Project/Step 2/MDR.v (/MDR_tb/test) - Default

```
// Zack Fravel
// System Synthesis and Modeling
// Final Project (Step 2)

module MDR(clk, reset, data_bus_in, data_bus_out, data_mem_in, data_mem_out, read_en, write_en, out_en);

// Input/Output/Register Declaration
input clk; input reset; input[15:0] data_mem_in; input[15:0] data_bus_in; input read_en; input write_en; input out_en;
output[15:0] data_mem_out; output tri[15:0] data_bus_out;

reg[15:0] read_data;
reg[15:0] write_data;

// Architecture
always@(posedge clk or posedge reset)
begin
    if (reset == 1)
    begin
        read_data <= 16'h0000;
        write_data <= 16'h0000;
    end
    else
        if(read_en == 1)
            read_data <= data_mem_in;
        else if(write_en == 1)
            write_data <= data_bus_in;
        end



    assign data_mem_out = write_data;
    assign data_bus_out = (out_en) ? read_data:16'hzzzz;
end

endmodule
```

```

1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Final Project (Step 2)
4
5 `timescale 1ns/1ns
6 module MDR_tb;
7
8 // Inputs
9     reg clk; reg reset; reg[15:0] dataBUS_in; reg[15:0] dataMEM_in; reg rEN; reg wEN; reg oEN;
10 // Outputs
11     wire dataBUS_out; wire dataMEM_out;
12 // Declare module
13     MDR test(clk, reset, dataBUS_in, dataBUS_out, dataMEM_in, dataMEM_out, rEN, wEN, oEN);
14 // Testbench
15
16     always #10 clk = ~clk;
17
18     initial
19     begin
20         clk = 0; reset = 0; dataBUS_in = 16'h0000;
21         dataMEM_in = 16'h0000; rEN = 0; wEN = 0; oEN = 0;
22
23         #20; reset = 1; #20; reset = 0;
24
25         #20; dataBUS_in = 16'h1101; dataMEM_in = 16'h0010;
26
27         #40; rEN = 1; #20; rEN = 0;
28
29         #20; oEN = 1; #20; oEN = 0;
30
31         #40; wEN = 1; #20; wEN = 0;
32
33     end
34



```

  

GPR

```
1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Final Project (Step 2)
4
5 module GPR(clk, reset, bus_in, inEn, outEn, bus_out);
6
7 // Input/Output/Register Declaration
8 input clk; input reset; input[15:0] bus_in; input inEn; input outEn;
9 output tri[15:0] bus_out;
10
11 reg[15:0] data;
12
13 // Architecture
14 always@(posedge clk or posedge reset)
15 begin
16     if (reset == 1)
17         data <= 16'h0000;
18     else
19         if(inEn == 1)
20             data <= bus_in;
21 end
22
23 assign bus_out = (outEn) ? data:16'hzzzz;
24
25 endmodule
```

```
1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Final Project (Step 2)
4
5 `timescale 1ns/1ns
6 module GPR_tb;
7
8 // Inputs
9     reg clk; reg reset; reg[15:0] from_bus; reg inEn; reg outEn;
10 // Outputs
11     wire to_bus;
12 // Declare module
13     GPR test(clk, reset, from_bus, inEn, outEn, to_bus);
14 // Testbench
15
16     always #10 clk = ~clk;
17
18     initial
19     begin
20         clk = 0; reset = 0; from_bus = 16'h0000; inEn = 0; outEn = 0;
21
22         #20; reset = 1; #20; reset = 0;
23
24         #40; from_bus = 16'h1111; #20; inEn = 1; #20 inEn = 0;
25
26         #20; outEn = 1; #20; outEn = 0;
27
28     end
29
30 endmodule
```

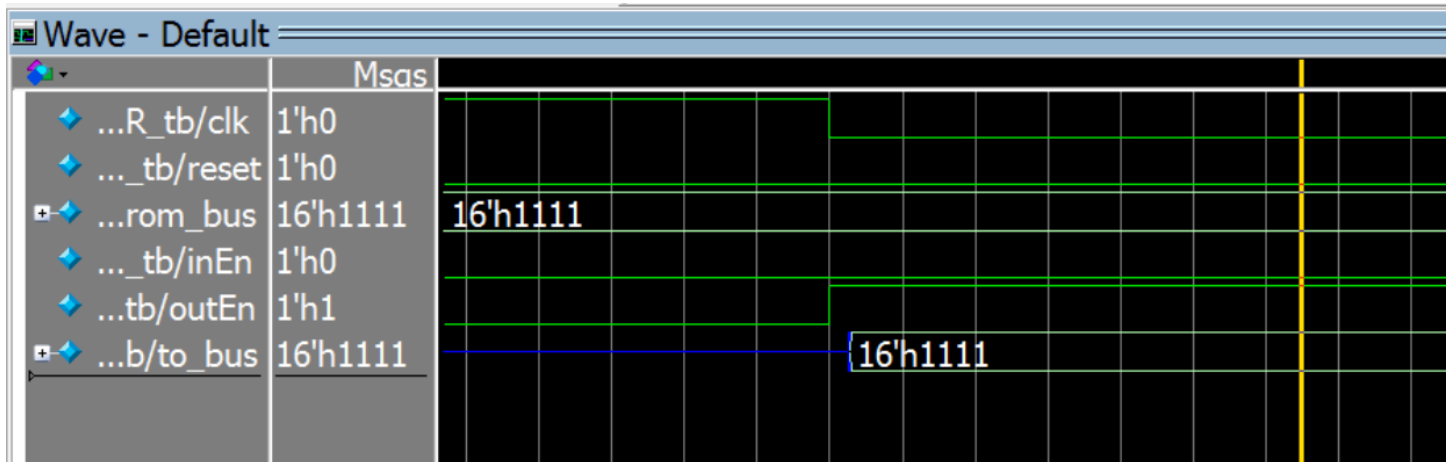 

Program Counter

```

1  // Zack Fravel
2  // System Synthesis and Modeling
3  // Final Project (Step 2)
4
5  module programCounter(clk, reset, increment, oTriEn, PC_out);
6
7  // Input/Output/Register Declaration
8  input clk; input reset; input increment;
9  input oTriEn; output tri[15:0] PC_out;
10 reg[15:0] counter;
11
12 // Architecture
13
14 always@(posedge clk or posedge reset)
15 begin
16
17     if(reset == 1)
18         counter <= 16'h0000;
19     else
20         if(increment == 1)
21             counter <= counter + 1;
22
23 end
24
25 assign PC_out = (oTriEn) ? counter:16'hzzzz;
26
27 endmodule

```

```

1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Final Project (Step 2)
4
5 `timescale 1ns/1ns
6 module programCounter_tb;
7
8 // Inputs
9     reg clk; reg reset; reg increment; reg oTriEn;
10 // Outputs
11     wire data_out;
12 // Declare module
13     programCounter test(clk, reset, increment, oTriEn, data_out);
14 // Testbench
15
16     always #10 clk = ~clk;
17
18     initial
19     begin
20         clk = 0; reset = 0; increment = 0; oTriEn = 0;
21         #20; reset = 1;
22         #20; reset = 0;
23         #20; increment = 1;
24         #20; increment = 0;
25         #20; oTriEn = 1;
26         #20; oTriEn = 0;
27         #20; increment = 1;
28         #100; increment = 0;
29         #20; oTriEn = 1;
30         #20; oTriEn = 0;
31
32     end
33
34 endmodule

```

