

Project 3

System Synthesis and Modeling

Zack Fravel

010646947

zpfravel@uark.edu

Introduction

The objective of Project 3 was to design and simulate a given combinational circuit in Verilog using ModelSim. Specifically, the circuit we want to design takes in an 8-bit input and counts the number of 1's detected in the word; after counting them up, the circuit then outputs the counter result using a 4 bit output. Similar to our previous projects, we were also tasked with not only implementing the solution in Verilog, but also writing a testbench or .DO file depending on our method of simulation. Finally, we also want to show the the circuit works as designed for all possible 8-bit input patterns.

Design and Simulation

The overarching idea of the assigned combinational circuit is shown below, in figure 1. To reiterate, we want to take in 8 bits at once and set a 4 bit output equal to the number of 1's detected in the 8 bit input.

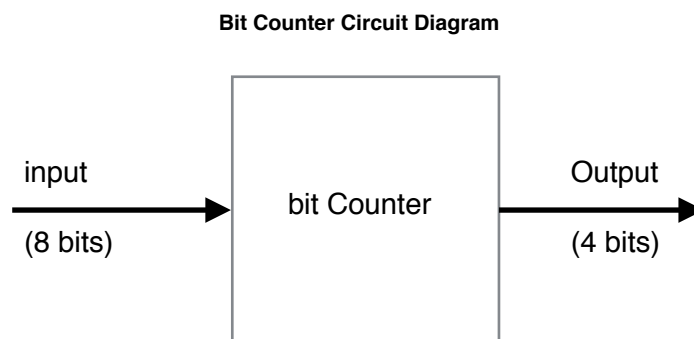


Figure 1

The implementation of this circuit in Verilog is very straight forward, we want to declare our input [7:0] and our output [3:0] (I declare them as wires since we don't need to store any data, just performing an operation). After our ports have been declared all that is needed is one line of code which assigns the output to the sum of each bit in the input stream. Below, in figure 2, is a

screenshot of the Verilog design.

bitCounter.v

```
Ln#
1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Project 3
4
5 module bitCounter(
6     input wire [7:0] in,
7     output wire [3:0] out
8 );
9
10 assign out = in[7] + in[6] + in[5] + in[4] + in[3] + in[2] + in[1] + in[0]; // Adds up all the 1's in the input
11
12 endmodule
```

Figure 2

Once I was sure it compiled correctly, I moved on to designing a suitable testbench to go through all possible combinations of input.

I declare the testbench module as bitCounter_tb and below declare reg [7:0] testIn, wire [3:0] testOut, and finally initialize my bitCounter module using the respective ports. At the top of the testbench I declare my timescale as 1ns/1ns to be able and add some delay between each operation. In my initial block I have the simulator wait 20ns and set the input to “00000000.” From here, I create a while loop that checks if the input is less than 256 (255 being the greatest possible integer value that can be stored in 8 bits). Within this while loop I have the compiler display the current state of the input and output; after that is complete the testbench increments the input by 1 and waits 5 ns. This repeats until the input reaches 255, and the cycle continues for as long as is needed. Attached also is figure 3, which shows the Verilog implementation of this testbench module.

bitCounter_tb.v


```
Ln#
1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Project 3
4
5 `timescale 1ns/1ns
6 module bitCounter_tb;
7
8 // Inputs
9     reg[7:0] testIn;
10 // Output
11     wire[3:0] testOut;
12 // Instantiate Module
13     bitCounter test (testIn, testOut);
14
15 // Testbench
16 initial
17
18     begin
19
20         #20; // Wait 20ns and assign input to all 0's
21         testIn = 8'b00000000;
22
23         while(testIn < 256)
24         begin
25             $display("input: ", testIn, "    output:", testOut);
26             testIn = testIn + 1;
27             #5;
28         end
29
30     end
31
32 endmodule
```

Figure 3

Results, Analysis, and Conclusions

Once I had my testbench compiled I was ready to begin simulating. I loaded the testbench into the simulator and added the testIn and testOut waves and ran for 1500ns, which is more than enough time for the testbench to run through all possible input patterns with a 5ns delay between each. Below are a three waveform screenshots of random points in the simulation run time.

Simulation

 

 


Figure 4

It can be seen above that the combinational circuit designed does exactly what we set out to do. In the first screenshot, we have an input “10101011,” which contains 5 “1” bits; on our output, we have 0101, which is the 4 bit representation for the number 5. On the second screenshot we show 8 bits that assert “1”, and on the third shows 4 bits with each having their correct output. The compiler also outputs a string each time it loops displaying the input and output, which is attached to the end of the report.

My simulation ran for 1500 ns, which was enough time for the circuit to go through all possible combinations, plus about 45 after being set back to “00000000.” I included some of the repeating in the output attached at the end, just to show it functions and loops correctly. In conclusion, I successfully designed a simple combinational circuit in Verilog that takes in 8-bits, counts the number of 1’s present, and outputs a 4-bit representation of that counter. All source files are included in the report package.

Compiler Output

```
# input: 0 output: 0
# input: 1 output: 1
# input: 2 output: 1
# input: 3 output: 2
# input: 4 output: 1
# input: 5 output: 2
# input: 6 output: 2
# input: 7 output: 3
# input: 8 output: 1
# input: 9 output: 2
# input: 10 output: 2
# input: 11 output: 3
# input: 12 output: 2
# input: 13 output: 3
# input: 14 output: 3
# input: 15 output: 4
# input: 16 output: 1
# input: 17 output: 2
# input: 18 output: 2
# input: 19 output: 3
# input: 20 output: 2
# input: 21 output: 3
# input: 22 output: 3
# input: 23 output: 4
# input: 24 output: 2
# input: 25 output: 3
# input: 26 output: 3
# input: 27 output: 4
# input: 28 output: 3
# input: 29 output: 4
# input: 30 output: 4
# input: 31 output: 5
# input: 32 output: 1
# input: 33 output: 2
# input: 34 output: 2
# input: 35 output: 3
# input: 36 output: 2
# input: 37 output: 3
# input: 38 output: 3
# input: 39 output: 4
# input: 40 output: 2
# input: 41 output: 3
# input: 42 output: 3
# input: 43 output: 4
# input: 44 output: 3
# input: 45 output: 4
# input: 46 output: 4
# input: 47 output: 5
# input: 48 output: 2
# input: 49 output: 3
# input: 50 output: 3
```

```
# input: 51 output: 4
# input: 52 output: 3
# input: 53 output: 4
# input: 54 output: 4
# input: 55 output: 5
# input: 56 output: 3
# input: 57 output: 4
# input: 58 output: 4
# input: 59 output: 5
# input: 60 output: 4
# input: 61 output: 5
# input: 62 output: 5
# input: 63 output: 6
# input: 64 output: 1
# input: 65 output: 2
# input: 66 output: 2
# input: 67 output: 3
# input: 68 output: 2
# input: 69 output: 3
# input: 70 output: 3
# input: 71 output: 4
# input: 72 output: 2
# input: 73 output: 3
# input: 74 output: 3
# input: 75 output: 4
# input: 76 output: 3
# input: 77 output: 4
# input: 78 output: 4
# input: 79 output: 5
# input: 80 output: 2
# input: 81 output: 3
# input: 82 output: 3
# input: 83 output: 4
# input: 84 output: 3
# input: 85 output: 4
# input: 86 output: 4
# input: 87 output: 5
# input: 88 output: 3
# input: 89 output: 4
# input: 90 output: 4
# input: 91 output: 5
# input: 92 output: 4
# input: 93 output: 5
# input: 94 output: 5
# input: 95 output: 6
# input: 96 output: 2
# input: 97 output: 3
# input: 98 output: 3
# input: 99 output: 4
# input: 100 output: 3
# input: 101 output: 4
# input: 102 output: 4
# input: 103 output: 5
# input: 104 output: 3
# input: 105 output: 4
# input: 106 output: 4
# input: 107 output: 5
# input: 108 output: 4
# input: 109 output: 5
# input: 110 output: 5
# input: 111 output: 6
# input: 112 output: 3
# input: 113 output: 4
# input: 114 output: 4
# input: 115 output: 5
```

```
# input: 116 output: 4
# input: 117 output: 5
# input: 118 output: 5
# input: 119 output: 6
# input: 120 output: 4
# input: 121 output: 5
# input: 122 output: 5
# input: 123 output: 6
# input: 124 output: 5
# input: 125 output: 6
# input: 126 output: 6
# input: 127 output: 7
# input: 128 output: 1
# input: 129 output: 2
# input: 130 output: 2
# input: 131 output: 3
# input: 132 output: 2
# input: 133 output: 3
# input: 134 output: 3
# input: 135 output: 4
# input: 136 output: 2
# input: 137 output: 3
# input: 138 output: 3
# input: 139 output: 4
# input: 140 output: 3
# input: 141 output: 4
# input: 142 output: 4
# input: 143 output: 5
# input: 144 output: 2
# input: 145 output: 3
# input: 146 output: 3
# input: 147 output: 4
# input: 148 output: 3
# input: 149 output: 4
# input: 150 output: 4
# input: 151 output: 5
# input: 152 output: 3
# input: 153 output: 4
# input: 154 output: 4
# input: 155 output: 5
# input: 156 output: 4
# input: 157 output: 5
# input: 158 output: 5
# input: 159 output: 6
# input: 160 output: 2
# input: 161 output: 3
# input: 162 output: 3
# input: 163 output: 4
# input: 164 output: 3
# input: 165 output: 4
# input: 166 output: 4
# input: 167 output: 5
# input: 168 output: 3
# input: 169 output: 4
# input: 170 output: 4
# input: 171 output: 5
# input: 172 output: 4
# input: 173 output: 5
# input: 174 output: 5
# input: 175 output: 6
# input: 176 output: 3
# input: 177 output: 4
# input: 178 output: 4
# input: 179 output: 5
# input: 180 output: 4
```

# input: 181	output: 5	# input: 231	output: 6
# input: 182	output: 5	# input: 232	output: 4
# input: 183	output: 6	# input: 233	output: 5
# input: 184	output: 4	# input: 234	output: 5
# input: 185	output: 5	# input: 235	output: 6
# input: 186	output: 5	# input: 236	output: 5
# input: 187	output: 6	# input: 237	output: 6
# input: 188	output: 5	# input: 238	output: 6
# input: 189	output: 6	# input: 239	output: 7
# input: 190	output: 6	# input: 240	output: 4
# input: 191	output: 7	# input: 241	output: 5
# input: 192	output: 2	# input: 242	output: 5
# input: 193	output: 3	# input: 243	output: 6
# input: 194	output: 3	# input: 244	output: 5
# input: 195	output: 4	# input: 245	output: 6
# input: 196	output: 3	# input: 246	output: 6
# input: 197	output: 4	# input: 247	output: 7
# input: 198	output: 4	# input: 248	output: 5
# input: 199	output: 5	# input: 249	output: 6
# input: 200	output: 3	# input: 250	output: 6
# input: 201	output: 4	# input: 251	output: 7
# input: 202	output: 4	# input: 252	output: 6
# input: 203	output: 5	# input: 253	output: 7
# input: 204	output: 4	# input: 254	output: 7
# input: 205	output: 5	# input: 255	output: 8
# input: 206	output: 5	# input: 0	output: 0
# input: 207	output: 6	# input: 1	output: 1
# input: 208	output: 3	# input: 2	output: 1
# input: 209	output: 4	# input: 3	output: 2
# input: 210	output: 4	# input: 4	output: 1
# input: 211	output: 5	# input: 5	output: 2
# input: 212	output: 4	# input: 6	output: 2
# input: 213	output: 5	# input: 7	output: 3
# input: 214	output: 5	# input: 8	output: 1
# input: 215	output: 6	# input: 9	output: 2
# input: 216	output: 4	# input: 10	output: 2
# input: 217	output: 5	# input: 11	output: 3
# input: 218	output: 5	# input: 12	output: 2
# input: 219	output: 6	# input: 13	output: 3
# input: 220	output: 5	# input: 14	output: 3
# input: 221	output: 6	# input: 15	output: 4
# input: 222	output: 6	# input: 16	output: 1
# input: 223	output: 7	# input: 17	output: 2
# input: 224	output: 3	# input: 18	output: 2
# input: 225	output: 4	# input: 19	output: 3
# input: 226	output: 4	# input: 20	output: 2
# input: 227	output: 5		
# input: 228	output: 4		
# input: 229	output: 5		
# input: 230	output: 5		

Figure 6