

System Synthesis and Modeling (CSCE 3953)

Project 6

Zack Fravel

10/19/16


zpfravel@uark.edu

Parent Objective

The parent objective of project six was to design and implement a finite state machine in verilog that acts as a race light controller. That is, we have a device that, upon initialization, cycles through red, yellow, and green lights. We want these lights to stay on for at least three clock cycles in our design. Once the controller cycles through the three colors it goes back to its initial state with only the red light being lit, which is also the reset state.

Design Methodology / STG

We were left to make our own assumptions in our design methodology for this project. For my design, I went with a Moore FSM. That is, a finite state machine whose outputs are totally dependent on only the current state. In order to ensure the lights stay on for at least three clock cycles after the start signal is introduced, I created three separate states for each light with each state transition set to happen on the positive edge of the clock. This ensures the lights stay on for three total clock cycles. Below is the state transition graph for my race light FSM.

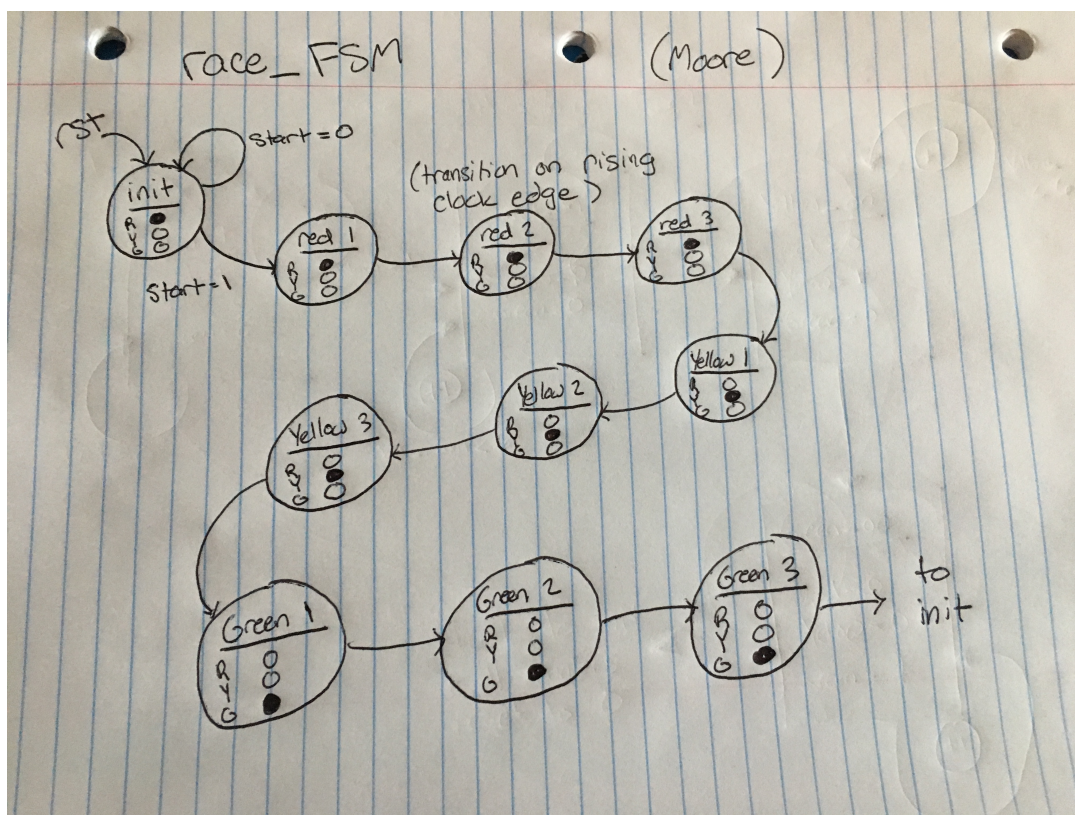

To implement this design in verilog, I created two four bit registers in order to store the current state and next state of the FSM and set parameters with their names respectively for all 10 states. (e.g. `init = 4'b0000`, `red_one = 4'b0001`, `red_two = 4'b0010...`) After that, the meat of the implementation went into three separate always blocks. The first always block is sensitive to the positive edge of the clock and the positive edge of the reset signal. This first block is responsible for handling the current state transition. If reset is high, the current state is set to “init” otherwise, the current state is set to whatever “next_state” is set to. The second always block handles the next state logic. This block is sensitive to the current state and start signals. Every time the current state changes from the first block, the second block runs and runs through a case statement to determine what the next state should be. In the init state, the circuit waits until the start signal is introduced and then sets the next state to red_one. After that, each state sets the next state to the one following it until at the very end green_three sets the next state back to init.

Finally, in the third always block I handle the outputs. This block is sensitive to the current state signal and contains a case statement for each case of current state. For each of the 10 states I set the outputs accordingly (e.g. `yellow_two: begin red <= 1'b0; yellow <= 1'b1; green <= 1'b0; end`). The source code for all the behavior described is included at the end of the report.

Simulation Method

For my simulation method I decided to write a testbench file. In my testbench I declare my inputs as registers and outputs as wires and instantiate my `race_FSM` module with the inputs and outputs I just declared. After that, I created an initial block that sets all three inputs (CLK,

RESET, and START) to 0 and wait 50 ns. I then set the reset signal to 1, wait 10 ns and set it back to 0. Then, after 20 ns I set the START signal to 1, wait 10 ns, and set it back to 0. Other than that, the only other thing in the testbench is an always statement that sets the CLK to its complement every 10 ns (20 ns period, 50 MHz).

To simulate the circuit with delay, I synthesized my design in Design Vision with the 90nm Standard Digital Cell Library. Once I compiled my design into the synthesis software I set my clock constraints with [create_clock -name "CLK_0" -period 50 -waveform {0.000 25.000} {clk}]. I then set the clock uncertainty and input/output delay exactly as I did in the previous project (0.14, 2.0, 0.5 respectively). Below is the timing analysis report I ran after synthesis.

```

Report.1 - Timing
*****
Report : timing
        -path full
        -delay max
        -max_paths 1
        -sort_by group
Design : race_FSM
Version: C-2009.06-SP2
Date   : Tue Oct 18 16:56:19 2016
*****

Operating Conditions: TYPICAL   Library: saed90nm_typ
Wire Load Model Mode: enclosed

Startpoint: red_reg (positive level-sensitive latch)
Endpoint: red (output port clocked by CLK_0)
Path Group: (none)
Path Type: max

Des/Clust/Port      Wire Load Model      Library
-----
race_FSM            8000                      saed90nm_typ




Point              Incr      Path
-----
red_reg/CLK (LATCHX2)      0.00      0.00 r
red_reg/Q (LATCHX2)       0.17      0.17 r
red (out)                 0.00      0.17 r
data arrival time                               0.17
-----
(Path is unconstrained)

***** End Of Report *****

```

Result

   The following is a screenshot of the simulation waveform of the behavioral code as well as the waveform for my synthesized design. Both are running the same testbench described in the previous section. After the two full simulation screenshots I include another zoomed in shot to show the gate delay on the state transition between “red_three” and “yellow_one.”



Analysis and Conclusion

Initially I ran into a number of issues trying to synthesize a design that relied on counters and the combinational part being sensitive to the clock. This caused no issues in the behavioral design however when I tried to synthesize the code I ran into a number of strange random number generation errors as well as slack timing not being met. Once I changed my design to rely solely on state transitions and no counters everything went smoothly. In conclusion, we ended up with exactly what we set out to design; we have a race light Moore finite state machine that, upon receiving a start signal, transitions out of its initial state and cycles through red, yellow, and green lights with each light staying on for three clock cycles and returning to the initial state after completion.

Source Code

```
X:/Windows/race_FSM.v - Default
Ln# 1503

1 // Zack Fravel
2 // System Synthesis and Modeling
3 // Project 6
4
5 `timescale 1ns/1ns
6 module race_FSM(
7     input wire clk,
8     input wire reset,
9     input wire start,
10    output reg red,
11    output reg yellow,
12    output reg green
13 );
14
15
16 reg[3:0] current_state, next_state; // State Signals
17
18 parameter init = 4'b0000, red_one = 4'b0001, red_two = 4'b0010, red_three = 4'b0011,
19    yellow_one = 4'b0100, yellow_two = 4'b0101, yellow_three = 4'b0110, // Set Parameters for State Signals
20    green_one = 4'b0111, green_two = 4'b1000, green_three = 4'b1001;
21
22
23 always @(posedge clk or posedge reset) // Current State Transition
24 begin
25     if(reset)
26         current_state <= init;
27     else
28         current_state <= next_state;
29 end
30
31
32
33 always @(current_state or start) // Next State Logic
34 begin
35
36     case(current_state)
37
38     init: begin
39         if(start)
40             next_state <= red_one;
41         else
42             next_state <= init;
43         end
44
45     red_one: begin next_state <= red_two; end
46     red_two: begin next_state <= red_three; end
47     red_three: begin next_state <= yellow_one; end
48
49     yellow_one: begin next_state <= yellow_two; end
50     yellow_two: begin next_state <= yellow_three; end
51     yellow_three: begin next_state <= green_one; end
52
53     green_one: begin next_state <= green_two; end
54     green_two: begin next_state <= green_three; end
55     green_three: begin next_state <= init; end
56
57     endcase
58 end
59
60 always @(current_state)
61 begin
62
63     case (current_state)
64
65     init: begin red <= 1'b1; yellow <= 1'b0; green <= 1'b0; end
66
67     red_one: begin red <= 1'b1; yellow <= 1'b0; green <= 1'b0; end
68     red_two: begin red <= 1'b1; yellow <= 1'b0; green <= 1'b0; end
69     red_three: begin red <= 1'b1; yellow <= 1'b0; green <= 1'b0; end
70
71     yellow_one: begin red <= 1'b0; yellow <= 1'b1; green <= 1'b0; end
72     yellow_two: begin red <= 1'b0; yellow <= 1'b1; green <= 1'b0; end
73     yellow_three: begin red <= 1'b0; yellow <= 1'b1; green <= 1'b0; end
74
75     green_one: begin red <= 1'b0; yellow <= 1'b0; green <= 1'b1; end
76     green_two: begin red <= 1'b0; yellow <= 1'b0; green <= 1'b1; end
77     green_three: begin red <= 1'b0; yellow <= 1'b0; green <= 1'b1; end
78
79     endcase
80
81 end
82
83 endmodule
```

X:/Windows/race_FSM_tb.v (/race_FSM_tb) - Default

Ln#	
1	// Zack Fravel
2	// System Synthesis and Modeling
3	// Project 6
4	
5	`timescale 1ns/1ns
6	module race_FSM_tb;
7	
8	// Inputs
9	reg CLK; reg RESET; reg START;
10	// Outputs
11	wire RED; wire YELLOW; wire GREEN;
12	// Instantiate Module
13	race_FSM syn (CLK, RESET, START, RED, YELLOW, GREEN);
14	
15	initial
16	begin
17	CLK = 0;
18	RESET = 0;
19	START = 0;
20	#50;
21	RESET = 1;
22	#10;
23	RESET = 0;
24	#20;
25	START = 1;
26	#10;
27	START = 0;
28	end
29	
30	always #10 CLK = ~CLK;
31	
32	endmodule